




Objective: Apply complex number operations to electrical circuit problems

Concept

Electrical engineers use complex numbers when analyzing electric circuits. An electric circuit commonly contains three types of components: resistors, inductors, and capacitors. As electrons flow through the circuit, each component affects the flow in a different way. The impedance (measured in ohms, Ω) is the resistance to the flow of electrons in an AC circuit.


The table shows the symbol used for each component in a circuit diagram, the phase angle, and the method for representing the impedance of that component as a complex number.

Circuit component	Symbol in circuit diagram	Phase angle	Representation by a complex number
Resistor		0°	A real number a
Inductor		90°	An imaginary number bi where $b > 0$
Capacitor		-90°	An imaginary number bi where $b < 0$

Objective: Apply complex number operations to electrical circuit problems

Ex) The diagram of an alternating current (AC) electric circuit is shown, with the impedance of each component. An AC power source, which is shown on the left and labeled 120 V (for volts), causes electrons to flow through the circuit.

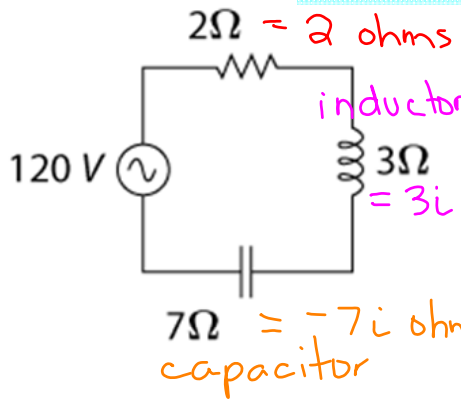resistor Represent the impedance of each component as a complex number.



a) Impedance of the capacitor = $-7i$ ohms.

b) Impedance of the resistor = 2 ohms.

c) Impedance of the inductor = $3i$ ohms.

d) The total impedance of a circuit is the sum of the impedances of its components. The total impedance of the AC circuit is $2 - 4i$ ohms.

Circuit component	Symbol in circuit diagram	Phase angle	Representation by a complex number
<u>Resistor</u>		0°	<u>A real number a</u>
<u>Inductor</u>		90°	<u>An imaginary number bi where $b > 0$</u>
Capacitor		-90°	<u>An imaginary number bi where $b < 0$</u>


total impedance
 $-7i + 2 + 3i$
 $2 - 4i$ ohms

Objective: Apply complex number operations to electrical circuit problems

Ex) Ohm's Law for electric circuits says that the voltage V (measured in volts) is the product of the current I (measured in amps) and the impedance Z (measured in ohms).

Ohm's Law

$$V = I \cdot Z$$

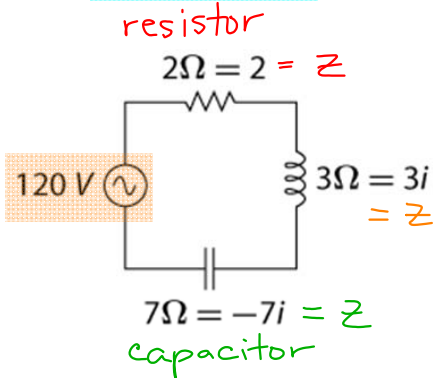

In the given circuit, the current I is $12 + 24i$ amps.

Calculate the voltage for each component of the circuit.

a) What is the voltage for the resistor?

$$V = I \cdot Z = (12 + 24i)2 = 2(12 + 24i) = 24 + 48i \text{ volts}$$

Voltage for the resistor is $24 + 48i$ volts

b) What is the voltage for the capacitor?

$$V = I \cdot Z = (12 + 24i)(-7i) = -7i(12 + 24i) = -84i - 168i^2 = 168 - 84i \text{ volts}$$

The voltage for the capacitor is $168 - 84i$ volts.

c) What is the voltage for the inductor?

$$V = I \cdot Z = (12 + 24i)3i = 3i(12 + 24i) = 36i + 72i^2 = -72 + 36i \text{ volts}$$

The voltage of the inductor is $-72 + 36i$ volts.

d) Find the sum of the voltages for the three components of the circuit. What do you notice?

$$\begin{array}{r} 24 + 48i + 168 - 84i + -72 + 36i \\ \hline 24 + 168 + -72 + 48i + -84i + 36i \\ 192 + -72 + 84i + -84i = 0 \end{array}$$

120 volts


The sum of the voltages for the three components equals the voltage of the circuit.

Objective: Apply complex number operations to electrical circuit problems

Ex) The current of the AC electric circuit in the diagram is measured as $6 + 4i$ amps.

A) What is the total impedance of the circuit?

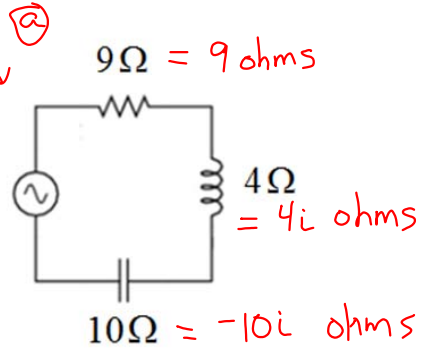B) What is the total voltage of the circuit?



Ⓐ total impedance
 $= 9 + 4i + -10i \text{ ohms}$
 $= 9 - 6i \text{ ohms}$

The total impedance of the circuit is $9 - 6i$ ohms.

Ⓑ Ohm's Law

Voltage = Current · Impedance

$V = I \cdot Z$

$V = (6 + 4i)(9 - 6i)$


$6(9 - 6i) + 4i(9 - 6i)$
 $54 - 36i + 36i - 24i^2$
 $+24 \leftarrow -24 \cdot -1$
 $= 78 \text{ volts}$

The total voltage of the circuit is 78 volts.

Objective: Apply complex number operations to electrical circuit problems

Ex) A second resistor is added to the circuit shown in the diagram. The second resistor has an impedance of 6 ohms.

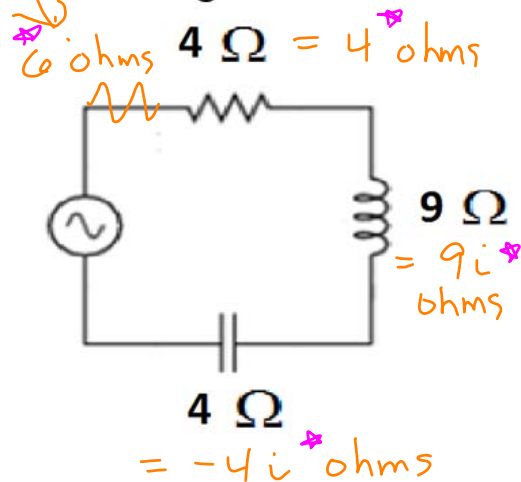- A) What is the total impedance of the circuit?
 B) If the current of the circuit is measured as $16 - 8i$ amps, what is the total voltage of the circuit?



(a) $6 + 4 + 9i + -4i = 10 + 5i \text{ ohms}$
 The total impedance is $10 + 5i \text{ ohms}$.

(b) $V = I \cdot Z$
 $V = (16 - 8i)(10 + 5i)$
 $= 160 + \cancel{80i} - \cancel{80i} - 40i^2$
 $= 200 \text{ volts}$

The total voltage is 200 volts.